

DESIGN AND IMPLEMENTATION OF A 32-BIT SINGLE-CYCLE RISC-V PROCESSOR


USING VERILOG HDL



SINGLE CYCLE
ARCHITECTURE



32-BIT
DATAPATH

 

SUPPORTS
RV32I
INSTRUCTIONS



VERIFIED BY
SIMULATION



Name : Radwa Mohamed Reda



Course : Digital Design



Course By : IEEE CUSB



IEEE

Single Cycle RV-32I Processor

Final Project

Table Of Content:

1. Introduction:	04
2. Project Objective:	04
1. Processor Specifications:	05
2. Supported Instructions:	06
3. Processor Architecture:	06
4. Modules Descriptions:	07
• Adder:	07
• Multiplexer:	08
• Program Counter:	08
• Instruction Memory:	10
• Register File:	11
• Sign Extension Unit:	12
• ALU:	13
• Data Memory:	14
• Main Decoder:	15
• ALU Decoder:	16
• Branch Decoder:	18
• Control Unit:	18
• Top Module:	20
5. Testbench:	24
6. Simulation & Results:	26
• Execution Transcript:	26
• Final Register File and Data Memory:	28
• Waveform Verification:	28
7. Conclusion:	29

Final Project

Introduction:

The Reduced Instruction Set Computer Version Five (RISC-V) is a modern open-source Instruction Set Architecture (ISA) designed to provide a simple, modular, and extensible processor architecture. Due to its flexibility and simplicity, RISC-V has become widely used in both academic and industrial applications for processor design and computer architecture education.

This project presents the implementation of a 32-bit Single-Cycle RISC-V Processor based on the Harvard Architecture, where the instruction memory and data memory are physically separated. In a single-cycle processor, every instruction is executed completely within a single clock cycle. Therefore, all stages of instruction execution—including instruction fetch, instruction decode, register read, execution, memory access, write-back, and program counter update—are completed before the next clock edge.

The processor was designed using Verilog Hardware Description Language (HDL) following a modular approach. Each hardware component was implemented as an independent module, including the Arithmetic Logic Unit (ALU), Program Counter, Instruction Memory, Register File, Data Memory, Control Unit, Sign Extension Unit, Multiplexers, Adders, and Next Program Counter Logic. These modules were then integrated into a top-level processor module to form a complete RISC-V implementation.

The processor supports a subset of the RISC-V instruction set, including arithmetic operations, logical operations, immediate instructions, memory access instructions (Load and Store), and branch instructions. The correctness of the design was verified through simulation using a testbench that executes a Fibonacci program stored in the instruction memory.

Objective:

The objective of this project is to design, implement, and verify a 32-bit Single-Cycle RISC-V Processor using Verilog HDL according to the provided processor datapath.

The processor is required to implement all major hardware modules of the RISC-V architecture, including the Program Counter, Instruction Memory, Register File, Arithmetic Logic Unit (ALU), Data Memory, Control Unit, Sign Extension Unit, Multiplexers, Adders, and Next Program Counter Logic. These modules are integrated into a top-level processor capable of executing instructions in a single clock cycle.

The implemented processor supports a subset of the RISC-V ISA consisting of:

- Arithmetic instructions
- Logical instructions

Final Project

- Immediate instructions
- Load Word (LW)
- Store Word (SW)
- Branch Equal (BEQ)
- Branch Not Equal (BNE)
- Branch Less Than (BLT)

Finally, the processor is verified through simulation by executing a Fibonacci program loaded into the instruction memory. The simulation results are compared with the expected output to ensure that all processor modules operate correctly and interact properly within the complete datapath

Processor Specifications:


FEATURE	VALUE
ISA	RV32I (subset)
DATAPATH WIDTH	32 bits
ARCHITECTURE	Single Cycle
REGISTER FILE	32 × 32-bit
INSTRUCTION MEMORY	64 × 32-bit
DATA MEMORY	64 × 32-bit
READ TYPE	Asynchronous
WRITE TYPE	Synchronous
BRANCHES	BEQ, BNE, BLT

Final Project

Supported Instructions:

CATEGORY	INSTRUCTIONS
ARITHMETIC	ADD, SUB
LOGICAL	AND, OR, XOR
SHIFT	SLL, SRL
IMMEDIATE	ADDI, SLLI
MEMORY	LW, SW
BRANCH	BEQ, BNE, BLT

Processor Architecture:

 

The processor consists of the following functional units:

- Program Counter
- Instruction Memory
- Register File
- Sign Extension Unit
- ALU

Final Project

- Data Memory
- Control Unit
- Next PC Logic
- Multiplexers

Modules Descriptions:

1. Adder:

```

/*
-----
Module Name : Adder_32B

Description :
- A 32-bit combinational adder used in the RISC-V processor.
- Adds two input operands (A and B).
- Produces the arithmetic sum on the output (Sum).
- Implemented using a continuous assignment statement.
- No clock or reset is required since the operation is purely combinational.
- Parameterized by WIDTH (default = 32 bits) for flexibility.
-----
*/

module Adder_32B #(
    parameter WIDTH = 32
) (
    input    wire    [WIDTH-1:0]    A,
    input    wire    [WIDTH-1:0]    B,
    output   wire    [WIDTH-1:0]    Sum
);

    assign Sum = A + B;

endmodule

```

2. Multiplexer:

```

/*
-----
-
Module Name : MUX_2X1

Description :
- A 2-to-1 multiplexer used in the RISC-V processor.
- Selects one of two input operands (A or B) based on the
  select signal (Sel).
- When Sel = 0, input A is forwarded to the output.
- When Sel = 1, input B is forwarded to the output.
- Implemented as a combinational logic block using an
  always @(*) statement.
- Parameterized by WIDTH (default = 32 bits) to support
  different data widths.
-----
-
*/

```

Final Project

```

module MUX_2X1 #(
    parameter WIDTH = 32
) (
    input      wire    [WIDTH-1:0]    A,
    input      wire    [WIDTH-1:0]    B,
    input      wire    Sel,
    output     reg     [WIDTH-1:0]    Y
);

always @(*) begin
    case(Sel)
        1'b0:    Y = A;
        1'b1:    Y = B;
        default: Y = {WIDTH{1'b0}};
    endcase
end

endmodule
```

```

## 3. Program Counter:

```

/*

-
Module Name : PC_Reg

Description :
- 32-bit Program Counter (PC) register.
- Stores the address of the current instruction.
- Loads the next program counter value (PCNext) on the
 rising
 edge of the clock when the load signal is asserted.
- Supports an active-low asynchronous reset that clears the
 program counter to zero.

-
*/

module PC_Reg #(
 parameter WIDTH = 32
) (
 input wire [WIDTH-1:0] PCNext,
 input wire load,
 input wire clk,
 input wire rst_n,
 output reg [WIDTH-1:0] PC
);

```



# Final Project

```

always @(posedge clk or negedge rst_n) begin
 if(!rst_n) begin
 PC <= {WIDTH{1'b0}};
 end else if(load) begin
 PC <= PCNext;
 end
end
endmodule

```

```

/*

-
Module Name : Next_PC_Calc

Description :
- Calculates the next value of the Program Counter (PC).
- Computes both PC + 4 and PC + ImmExt.
- Uses the PCSrc control signal to select the appropriate
 next PC value.
- PC + 4 is used for sequential execution, while PC +
 ImmExt
 is used for branch instructions.

-
*/

module Next_PC_Calc #(
 parameter WIDTH = 32
) (
 input wire [WIDTH-1:0] PC,
 input wire [WIDTH-1:0] ImmExt,
 input wire PCSrc,
 output wire [WIDTH-1:0] PCNext
);

wire [WIDTH-1:0] PCTarget;
wire [WIDTH-1:0] PCPlus4;

localparam [WIDTH-1:0] FOUR = 32'd4;

Adder_32B #(
 .WIDTH(WIDTH)
) PC_Target_Adder (
 .A(PC),
 .B(ImmExt),
 .Sum(PCTarget)
);

Adder_32B #(
 .WIDTH(WIDTH)
) PCPlus4_Adder (
 .A(PC),
 .B(FOUR),
 .Sum(PCPlus4)
);

```

# Final Project

```
MUX_2X1 #(
 .WIDTH(WIDTH)
) PC_Select_MUX (
 .A(PCPlus4),
 .B(PCTarget),
 .Sel(PCSrc),
 .Y(PCNext)
);
endmodule
```

## 4. Instruction Memory

```
/*

Module Name : Instruction_Memory

Description :
- Read-only memory (ROM) used to store program instructions.
- Provides asynchronous read access.
- Stores 64 instructions, each 32 bits wide.
- The Program Counter (PC) is connected directly to the
 address input.
- Memory is word-aligned; therefore, address bits [31:2]
 are used to index the ROM.

 Byte Address:
 0 4 8 12 16 20 24 28 32

 ROM Index:
 0 1 2 3 4 5 6 7 8

*/

module Instruction_Memory #(
 parameter WIDTH = 32,
 parameter DEPTH = 64,
 parameter ADDR_WIDTH = $clog2(DEPTH)
) (
 input wire [WIDTH-1:0] A, // 32-bit Program Counter
 address
 output wire [WIDTH-1:0] RD // Instruction output
);

reg [WIDTH-1:0] ROM [0:DEPTH-1];

// Asynchronous read access
assign RD = ROM[A[ADDR_WIDTH+1:2]]; // Ignore bits [1:0] for word alignment

endmodule
```

# Final Project

## 5. Register File

```

/*

Module Name : Reg_File

Description :
- A register file used in the RISC-V processor.
- Contains 32 registers, each with 32-bit width.
- Provides two asynchronous read ports (RD1 and RD2).
- Provides one synchronous write port (WD3).
- The register data is written on the rising edge of the clock
 when the write enable signal (WE3) is high.
- Supports simultaneous reading from two registers and writing
 to one register.
- Register x0 is always read as zero according to RISC-V standard.

*/

module Reg_File #(
 parameter WIDTH = 32,
 parameter DEPTH = 32,
 parameter ADDR_WIDTH = $clog2(DEPTH)
) (
 input wire [ADDR_WIDTH-1:0] A1, // Address of the first register to read
 input wire [ADDR_WIDTH-1:0] A2, // Address of the second register to read
 input wire [ADDR_WIDTH-1:0] A3, // Address of the register to write
 input wire [WIDTH-1:0] WD3, // Data to write to the register file
 input wire clk,
 input wire rst_n,
 input wire WE3, // Write Enable for the register file
 output reg [WIDTH-1:0] RD1, // Data read from the first registers
 output reg [WIDTH-1:0] RD2, // Data read from the second registers
);

reg [WIDTH-1:0] RAM [0:DEPTH-1]; // Register file array

// write synchronously
integer i;

always @(posedge clk or negedge rst_n) begin
 if(!rst_n) begin
 for(i=0;i<DEPTH;i=i+1)
 RAM[i] <= 0;
 end
 else if(WE3 && (A3!=0))
 RAM[A3] <= WD3;
 end

// read asynchronously
always @(*) begin
 RD1 = (A1 == 0) ? {WIDTH{1'b0}} : RAM[A1];
 RD2 = (A2 == 0) ? {WIDTH{1'b0}} : RAM[A2];
end
endmodule

```

# Final Project

## 6. Sign Extend

```

/*

Module Name : signExtend

Description :
- Extracts the immediate field from the 32-bit instruction.
- Supports different immediate formats based on the instruction type
 (I-Type, S-Type and B-Type).
- Performs sign extension to convert the extracted immediate into a
 32-bit signed value.
- The immediate extraction mode is selected using the ImmSrc control signal
 generated by the Main Decoder.

*/

module signExtend #(
 parameter INSTR_WIDTH = 32,
 parameter IMM_WIDTH = 32
) (
 input wire [INSTR_WIDTH - 1:7] Instr, // 32-bit instruction
 input wire [1:0] ImmSrc, // Immediate source selector
 output reg [IMM_WIDTH - 1:0] ImmExt // 32-bit sign-extended immediate
);

always @(*) begin

 case(ImmSrc)
 2'b00: ImmExt = {{20{Instr[31]}}, Instr[31:20]}; // I-Type & Load Instructions
 2'b01: ImmExt = {{20{Instr[31]}}, Instr[31:25], Instr[11:7]}; // S-Type
 2'b10: ImmExt = {
 {19{Instr[31]}},
 Instr[31],
 Instr[7],
 Instr[30:25],
 Instr[11:8],
 1'b0
 }; // B-Type
 default: ImmExt = {IMM_WIDTH{1'b0}}; // Default case
 endcase

end

endmodule

```

# Final Project

## 7. ALU

```

module ALU_32B #(
 parameter WIDTH = 32
) (
 input wire [WIDTH-1:0] SrcA,
 input wire [WIDTH-1:0] SrcB,
 input wire [2:0] ALUControl,

 output wire Zero,
 output wire SignFlag,
 output reg [WIDTH-1:0] ALUResult
);

always @(*) begin

 case(ALUControl)
 3'b000: ALUResult = SrcA + SrcB; // Addition
 3'b001: ALUResult = SrcA << SrcB[4:0]; // shift left logical
 3'b010: ALUResult = SrcA - SrcB; // Subtraction
 3'b100: ALUResult = SrcA ^ SrcB; // XOR
 3'b101: ALUResult = SrcA >> SrcB[4:0]; // shift right logical
 3'b110: ALUResult = SrcA | SrcB; // OR
 3'b111: ALUResult = SrcA & SrcB; // AND
 default: ALUResult = {WIDTH{1'b0}}; // NOP
 endcase

end

assign Zero = (ALUResult == {WIDTH{1'b0}});
assign SignFlag = ALUResult[WIDTH-1];
endmodule

```

# Final Project

## 8. Data Memory

```

/*

Module Name : Data_Memory

Description :
- A data memory module used in the RISC-V processor.
- Implements a single read/write memory port.
- Supports asynchronous read operation and synchronous write
 operation on the rising edge of the clock.
- Data is written to address A when Write Enable (WE) is high.
- The memory stores 64 entries, each with a 32-bit word width.
- The address input A is 32-bit, matching the processor datapath.
- Word-aligned addressing is used, where address bits [7:2]
 are used to access the 64 memory locations.
- The read data output (RD) is available without waiting for
 a clock edge.

*/

module Data_Memory #(
 parameter WIDTH = 32,
 parameter DEPTH = 64
) (
 input wire [WIDTH-1:0] A,
 input wire [WIDTH-1:0] WD,
 input wire WE,
 input wire clk,
 input wire rst_n,
 output wire [WIDTH-1:0] RD
);

reg [WIDTH-1:0] mem [0:DEPTH-1]; // Memory array

integer i;

always @(posedge clk or negedge rst_n) begin
 if(!rst_n) begin
 for(i=0; i<DEPTH; i=i+1)
 mem[i] <= 0;
 end
 else if(WE)
 mem[A[7:2]] <= WD;
 end

 assign RD = mem[A[7:2]]; // Asynchronous read access

endmodule

```



# Final Project

## 9. Main Decoder

```

/*

Module Name : Main_Decoder

Description :
- Decodes the 7-bit instruction opcode to generate the main
 control signals for the RISC-V processor.
- Implements combinational logic using a case statement.
- Supports the following instruction types:
 * Load Word (LW)
 * Store Word (SW)
 * R-Type instructions
 * I-Type instructions
 * Branch instructions
- Generates the following control signals:
 * RegWrite
 * ImmSrc
 * ALUSrc
 * MemWrite
 * ResultSrc
 * Branch
 * ALUOp
- Unsupported opcodes generate safe default control signals.

*/

module Main_Decoder (
 input wire [6:0] Opcode,

 output reg [1:0] ImmSrc,
 output reg Branch,
 output reg Load,
 output reg ResultSrc,
 output reg MemWrite,
 output reg ALUSrc,
 output reg RegWrite,
 output reg [1:0] ALUOp
);

 // Opcode definitions
 localparam LW = 7'b00000011; // Load Word
 localparam SW = 7'b0100011; // Store Word
 localparam R_TYPE = 7'b0110011; // R-Type instructions
 localparam I_TYPE = 7'b0010011; // I-Type instructions
 localparam BRANCH = 7'b1100011; // Branch instructions

 // Main Decoder Logic
 always @(*) begin
 // Default control signal values
 ImmSrc = 2'b00;
 Branch = 1'b0;
 Load = 1'b1; // Enable instruction/data access for all valid
 opcodes
 ResultSrc = 1'b0;
 MemWrite = 1'b0;
 ALUSrc = 1'b0;
 RegWrite = 1'b0;
 ALUOp = 2'b00;

 case (Opcode)
 LW: begin
 ImmSrc = 2'b00; // I-Type immediate
 ResultSrc = 1'b1; // Select memory data as result
 ALUSrc = 1'b1; // Use immediate for ALU operation
 RegWrite = 1'b1; // Enable register write
 ALUOp = 2'b00; // ALU performs addition for address
 calculation
 end
 end

```

# Final Project

```

 R_TYPE: begin
 RegWrite = 1'b1; // Enable register write
 ALUOp = 2'b10; // ALU operation determined by funct3
 and funct7 fields
 end

 I_TYPE: begin
 ImmSrc = 2'b00; // I-Type immediate
 RegWrite = 1'b1; // Enable register write
 ALUSrc = 1'b1; // Use immediate for ALU operation
 ALUOp = 2'b10; // ALU operation determined by funct3
 field (I-Type)
 end

 BRANCH: begin
 ImmSrc = 2'b10; // B-Type immediate
 Branch = 1'b1; // Enable branch operation
 ALUOp = 2'b01; // ALU performs subtraction
 end
 default: begin
 // Default case for unsupported opcodes
 ImmSrc = 2'b00;
 Branch = 1'b0;
 Load = 1'b0; // Disable load for unsupported opcodes
 ResultSrc = 1'b0;
 MemWrite = 1'b0;
 ALUSrc = 1'b0;
 RegWrite = 1'b0;
 ALUOp = 2'b00; // Default to addition
 end
 endcase
end
endmodule

```

## 10. ALU Decoder

```

/*

Module Name : ALU_Decoder

Description :
- Generates the ALU control signal based on:
 * ALUOp from the Main Decoder.
 * funct3 field.
 * Instr[30] (funct7 bit 5).
- Implements combinational logic.
- Supports the following ALU operations:
 * ADD
 * SUB
 * Shift Left Logical (SLL)
 * Shift Right Logical (SRL)
 * XOR
 * OR
 * AND
- For memory instructions (lw, sw), the ALU performs addition.
- For branch instructions, the ALU performs subtraction for
 comparison.
- Unsupported combinations default to the ADD operation.

*/

```

# Final Project

```

module ALU_Decoder (
 input wire [1:0] ALUOp,
 input wire [2:0] funct3, //instr[14:12]
 input wire Op5, // Opcode[5]
 input wire funct7_5, //instr[30]
 output reg [2:0] ALUControl
);

 // ALU operation codes
 localparam ADD = 3'b000;
 localparam SHL = 3'b001;
 localparam SUB = 3'b010;
 localparam XOR = 3'b100;
 localparam SHR = 3'b101;
 localparam OR = 3'b110;
 localparam AND = 3'b111;

 always @(*) begin
 ALUControl = ADD;

 case (ALUOp)
 2'b00: ALUControl = ADD; // For lw and sw instructions
 2'b01: ALUControl = SUB; // For branch instructions
 2'b10: begin // R-Type and I-Type instructions
 case (funct3)
 3'b000: ALUControl = (Op5 && funct7_5) ? SUB : ADD; // ADD or SUB
 3'b001: ALUControl = SHL; // Shift Left Logical
 3'b100: ALUControl = XOR; // XOR
 3'b101: ALUControl = SHR; // Shift Right Logical
 3'b110: ALUControl = OR; // OR
 3'b111: ALUControl = AND; // AND
 default: ALUControl = ADD; // Default to ADD for unsupported funct3 values
 endcase
 end
 default: ALUControl = ADD; // Default to ADD for unsupported ALUOp values
 endcase
 end

endmodule

```

# Final Project

## 11. Branch Decoder

```

/*

Branch Decision Logic

Description :
- Determines whether a branch should be taken.
- Uses the Branch control signal from the Main Decoder together
 with the ALU status flags.
- The branch operation is selected using the funct3 field.
- Supported branch instructions:
 * BEQ : Branch if Zero flag is asserted.
 * BNE : Branch if Zero flag is deasserted.
 * BLT : Branch if Sign flag is asserted.
- Implemented using a case statement controlled by funct3.

*/

module Branch_Decoder (
 input wire [2:0] funct3, //instr[14:12]
 input wire Zero, // ALU Zero flag
 input wire Sign_Flag, // ALU Sign flag
 input wire Branch, // Branch control signal from Main Decoder
 output reg PCSrc // Program Counter Source signal
);

always @(*) begin
 PCSrc = 1'b0; // Default to not taking the branch
 case (funct3)
 3'b000: PCSrc = Branch & Zero; // BEQ: Branch if Zero flag is asserted
 3'b001: PCSrc = Branch & ~Zero; // BNE: Branch if Zero flag is deasserted
 3'b100: PCSrc = Branch & Sign_Flag; // BLT: Branch if Sign flag is asserted
 default: PCSrc = 1'b0;
 endcase
end
endmodule

```

## 12. Control Unit

```

module Control_Unit (
 input wire [6:0] Opcode,
 input wire [2:0] Funct3,
 input wire Funct7_5,
 input wire zero,
 input wire Sign_Flag,

```

# Final Project

```

 output wire [1:0] ImmSrc,
 output wire Branch,
 output wire Load,
 output wire ResultSrc,
 output wire MemWrite,
 output wire ALUSrc,
 output wire RegWrite,
 output wire [2:0] ALUControl,
 output wire PCSrc
);

 wire [1:0] ALUOp;
 wire Op5;

 assign Op5 = Opcode[5];

 Main_Decoder main_decoder_inst (
 .Opcode(Opcode),
 .ImmSrc(ImmSrc),
 .Branch(Branch),
 .Load(Load),
 .ResultSrc(ResultSrc),
 .MemWrite(MemWrite),
 .ALUSrc(ALUSrc),
 .RegWrite(RegWrite),
 .ALUOp(ALUOp)
);

 ALU_Decoder alu_decoder_inst (
 .ALUOp(ALUOp),
 .funct3(Funct3),
 .Op5(Op5),
 .funct7_5(Funct7_5),
 .ALUControl(ALUControl)
);

 Branch_Decoder branch_decoder_inst (
 .funct3(Funct3),
 .Branch(Branch),
 .Zero(zero),
 .Sign_Flag(Sign_Flag),
 .PCSrc(PCSrc)
);

endmodule

```

# Final Project

## 13. RISC\_V\_Top

```

module RISC_V_Top #(
 parameter WIDTH = 32,
 parameter DEPTH = 64,
 parameter ADDR_WIDTH = $clog2(DEPTH)
) (
 input wire clk,
 input wire rst_n
);

////////////////////////////////////
////////////////////////////////////
// internal Sign_Flagals
////////////////////////////////////
////////////////////////////////////

wire [WIDTH-1:0] PC;
wire [WIDTH-1:0] PCNext;
wire [WIDTH-1:0] Instr;

wire [WIDTH-1:0] RD1;
wire [WIDTH-1:0] RD2;

wire [WIDTH-1:0] ImmExt;

wire [WIDTH-1:0] SrcB;

wire [WIDTH-1:0] ALUResult;

wire Zero;
wire Sign_Flag;

wire [WIDTH-1:0] ReadData;

wire [WIDTH-1:0] Result;

```

# Final Project

```

////////////////////////////////////
////////////////////////////////////
// Control Sign_Flags
////////////////////////////////////
////////////////////////////////////

wire RegWrite;
wire ALUSrc;
wire MemWrite;
wire ResultSrc;
wire Branch;
wire PCSrc;
wire Load;

wire [1:0] ImmSrc;
wire [2:0] ALUControl;

////////////////////////////////////
////////////////////////////////////
// Module Instantiations
////////////////////////////////////
////////////////////////////////////

Next_PC_Calc #(
 .WIDTH(WIDTH)
) Next_PC (
 .PC(PC),
 .ImmExt(ImmExt),
 .PCSrc(PCSrc),
 .PCNext(PCNext)
);

PC_Reg #(
 .WIDTH(WIDTH)
) PC_Register (
 .PCNext(PCNext),
 .load(1'b1), // Always load the next PC value
 .clk(clk),
 .rst_n(rst_n),
 .PC(PC)
);

Instruction_Memory #(
 .WIDTH(WIDTH),
 .DEPTH(DEPTH),
 .ADDR_WIDTH(ADDR_WIDTH)
) Instruction_Mem (
 .A(PC),
 .RD(Instr)
);

```

# Final Project

```

Reg_File #(
 .WIDTH(WIDTH),
 .DEPTH(32)
) Register_File (
 .clk(clk),
 .rst_n(rst_n),
 .WE3(RegWrite),
 .A1(Instr[19:15]),
 .A2(Instr[24:20]),
 .A3(Instr[11:7]),
 .WD3(Result),
 .RD1(RD1),
 .RD2(RD2)
);

MUX_2X1 #(
 .WIDTH(WIDTH)
) ALUSrc_MUX (
 .A(RD2),
 .B(ImmExt),
 .Sel(ALUSrc),
 .Y(SrcB)
);

ALU_32B #(
 .WIDTH(WIDTH)
) ALU (
 .SrcA(RD1),
 .SrcB(SrcB),
 .ALUControl(ALUControl),
 .ALUResult(ALUResult),
 .Zero(Zero),
 .SignFlag(Sign_Flag)
);

Data_Memory #(
 .WIDTH(WIDTH),
 .DEPTH(DEPTH)
) Data_Mem (
 .A(ALUResult),
 .WD(RD2),
 .WE(MemWrite),
 .clk(clk),
 .rst_n(rst_n),
 .RD(ReadData)
);

```



# Final Project

```

MUX_2X1 #(
 .WIDTH(WIDTH)
) ResultSrc_MUX (
 .A(ALUResult),
 .B(ReadData),
 .Sel(ResultSrc),
 .Y(Result)
);

Control_Unit Control (
 .Opcode(Instr[6:0]),
 .Funct3(Instr[14:12]),
 .Funct7_5(Instr[30]),
 .zero(Zero),
 .Sign_Flag(Sign_Flag),
 .RegWrite(RegWrite),
 .ALUSrc(ALUSrc),
 .MemWrite(MemWrite),
 .ResultSrc(ResultSrc),
 .Branch(Branch),
 .PCSrc(PCSrc),
 .ImmSrc(ImmSrc),
 .ALUControl(ALUControl),
 .Load(Load)
);

signExtend #(
 .INSTR_WIDTH(WIDTH),
 .IMM_WIDTH(WIDTH)
) Sign_Ext (
 .Instr(Instr[31:7]),
 .ImmSrc(ImmSrc),
 .ImmExt(ImmExt)
);

endmodule

```

# Final Project

## Testbench:

```

 `timescale 1ns/1ps

 module RISCv_Top_tb;

 reg clk;
 reg rst_n;
 integer i;

 //=====
 // Instantiate DUT
 //=====
 RISCv_Top DUT (
 .clk(clk),
 .rst_n(rst_n)
);

 //=====
 // Clock Generation
 //=====
 always #5 clk = ~clk;

 //=====
 // Initialization
 //=====
 initial begin
 clk = 0;
 rst_n = 0;

 // Load Program
 $readmemh("program.txt",
 DUT.Instruction_Mem.ROM);

 #20;
 rst_n = 1;
 end

```

# Final Project

```
//=====
=
// Monitor
//=====
=
initial begin
 $monitor(
 "t=%0t | PC=%h | Instr=%h | RD1=%0d | RD2=%0d |
Imm=%0d | ALUCtrl=%b | ALU=%0d | Result=%0d | Zero=%b
| Branch=%b | PCSrc=%b",
 $time,
 DUT.PC,
 DUT.Instr,
 $signed(DUT.RD1),
 $signed(DUT.RD2),
 $signed(DUT.ImmExt),
 DUT.ALUControl,
 $signed(DUT.ALUResult),
 $signed(DUT.Result),
 DUT.Zero,
 DUT.Branch,
 DUT.PCSrc
);
end

//=====
=
// Print Final Results
//=====
=
initial begin

 #1000;

 $display("\n=====")
;
 $display(" Final Register File");

 $display("=====");

 for(i=0;i<8;i=i+1)
 $display("x%0d = %0d", i,
DUT.Register_File.RAM[i]);

 $display("\n=====")
;
 $display(" Final Data Memory");

 $display("=====");

 for(i=0;i<10;i=i+1)
 $display("MEM[%0d] = %0d", i,
DUT.Data_Mem.mem[i]);

 $display("\n=====")
;

 $stop;

end

endmodule
```

# Final Project

## Simulation & Results:

### 1. Execution Transcript

| Transcript |             |                |        |        |          |             |        |           |        |          |         |  |
|------------|-------------|----------------|--------|--------|----------|-------------|--------|-----------|--------|----------|---------|--|
| # t=0      | PC=00000000 | Instr=00004033 | RD1=0  | RD2=0  | Imm=0    | ALUCtrl=100 | ALU=0  | Result=0  | Zero=1 | Branch=0 | PCSrc=0 |  |
| # t=25000  | PC=00000004 | Instr=00000093 | RD1=0  | RD2=0  | Imm=0    | ALUCtrl=000 | ALU=0  | Result=0  | Zero=1 | Branch=0 | PCSrc=0 |  |
| # t=35000  | PC=00000008 | Instr=00100113 | RD1=0  | RD2=0  | Imm=1    | ALUCtrl=000 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=45000  | PC=0000000c | Instr=00100193 | RD1=0  | RD2=0  | Imm=1    | ALUCtrl=000 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=55000  | PC=00000010 | Instr=00100213 | RD1=0  | RD2=0  | Imm=1    | ALUCtrl=000 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=65000  | PC=00000014 | Instr=00000293 | RD1=0  | RD2=0  | Imm=0    | ALUCtrl=000 | ALU=0  | Result=0  | Zero=1 | Branch=0 | PCSrc=0 |  |
| # t=75000  | PC=00000018 | Instr=00a00313 | RD1=0  | RD2=0  | Imm=10   | ALUCtrl=000 | ALU=10 | Result=10 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=85000  | PC=0000001c | Instr=00000393 | RD1=0  | RD2=0  | Imm=0    | ALUCtrl=000 | ALU=0  | Result=0  | Zero=1 | Branch=0 | PCSrc=0 |  |
| # t=95000  | PC=00000020 | Instr=00418c63 | RD1=1  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=105000 | PC=00000038 | Instr=002080b3 | RD1=0  | RD2=1  | Imm=2    | ALUCtrl=000 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=115000 | PC=0000003c | Instr=004181b3 | RD1=1  | RD2=1  | Imm=4    | ALUCtrl=000 | ALU=2  | Result=2  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=125000 | PC=00000040 | Instr=00229393 | RD1=0  | RD2=1  | Imm=2    | ALUCtrl=001 | ALU=0  | Result=0  | Zero=1 | Branch=0 | PCSrc=0 |  |
| # t=135000 | PC=00000044 | Instr=0013a023 | RD1=0  | RD2=1  | Imm=0    | ALUCtrl=000 | ALU=0  | Result=0  | Zero=1 | Branch=0 | PCSrc=0 |  |
| # t=145000 | PC=00000048 | Instr=00128293 | RD1=0  | RD2=1  | Imm=1    | ALUCtrl=000 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=155000 | PC=0000004c | Instr=fc62cae3 | RD1=1  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-9 | Result=-9 | Zero=0 | Branch=1 | PCSrc=1 |  |
| # t=165000 | PC=00000050 | Instr=00418c63 | RD1=2  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=1 | PCSrc=0 |  |
| # t=175000 | PC=00000054 | Instr=00110133 | RD1=1  | RD2=1  | Imm=1    | ALUCtrl=000 | ALU=2  | Result=2  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=185000 | PC=00000058 | Instr=404181b3 | RD1=2  | RD2=1  | Imm=1028 | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=195000 | PC=0000005c | Instr=00229393 | RD1=1  | RD2=2  | Imm=2    | ALUCtrl=001 | ALU=4  | Result=4  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=205000 | PC=00000060 | Instr=0023a023 | RD1=4  | RD2=2  | Imm=0    | ALUCtrl=000 | ALU=4  | Result=4  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=215000 | PC=00000064 | Instr=00420a63 | RD1=1  | RD2=1  | Imm=20   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=225000 | PC=00000068 | Instr=00128293 | RD1=1  | RD2=1  | Imm=1    | ALUCtrl=000 | ALU=2  | Result=2  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=235000 | PC=0000006c | Instr=fc62cae3 | RD1=2  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-8 | Result=-8 | Zero=0 | Branch=1 | PCSrc=1 |  |
| # t=245000 | PC=00000070 | Instr=00418c63 | RD1=1  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=255000 | PC=00000074 | Instr=002080b3 | RD1=1  | RD2=2  | Imm=2    | ALUCtrl=000 | ALU=3  | Result=3  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=265000 | PC=00000078 | Instr=004181b3 | RD1=1  | RD2=1  | Imm=4    | ALUCtrl=000 | ALU=2  | Result=2  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=275000 | PC=0000007c | Instr=00229393 | RD1=2  | RD2=2  | Imm=2    | ALUCtrl=001 | ALU=8  | Result=8  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=285000 | PC=00000080 | Instr=0013a023 | RD1=8  | RD2=3  | Imm=0    | ALUCtrl=000 | ALU=8  | Result=8  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=295000 | PC=00000084 | Instr=00128293 | RD1=2  | RD2=3  | Imm=1    | ALUCtrl=000 | ALU=3  | Result=3  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=305000 | PC=00000088 | Instr=fc62cae3 | RD1=3  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-7 | Result=-7 | Zero=0 | Branch=1 | PCSrc=1 |  |
| # t=315000 | PC=0000008c | Instr=00418c63 | RD1=2  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=1 | PCSrc=0 |  |
| # t=325000 | PC=00000090 | Instr=00110133 | RD1=2  | RD2=3  | Imm=1    | ALUCtrl=000 | ALU=5  | Result=5  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=335000 | PC=00000094 | Instr=404181b3 | RD1=2  | RD2=1  | Imm=1028 | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=345000 | PC=00000098 | Instr=00229393 | RD1=3  | RD2=5  | Imm=2    | ALUCtrl=001 | ALU=12 | Result=12 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=355000 | PC=0000009c | Instr=0023a023 | RD1=12 | RD2=5  | Imm=0    | ALUCtrl=000 | ALU=12 | Result=12 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=365000 | PC=000000a0 | Instr=00420a63 | RD1=1  | RD2=1  | Imm=20   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=375000 | PC=000000a4 | Instr=00128293 | RD1=3  | RD2=3  | Imm=1    | ALUCtrl=000 | ALU=4  | Result=4  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=385000 | PC=000000a8 | Instr=fc62cae3 | RD1=4  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-6 | Result=-6 | Zero=0 | Branch=1 | PCSrc=1 |  |
| # t=395000 | PC=000000ac | Instr=00418c63 | RD1=1  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=405000 | PC=000000b0 | Instr=002080b3 | RD1=3  | RD2=5  | Imm=2    | ALUCtrl=000 | ALU=8  | Result=8  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=415000 | PC=000000b4 | Instr=004181b3 | RD1=1  | RD2=1  | Imm=4    | ALUCtrl=000 | ALU=2  | Result=2  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=425000 | PC=000000b8 | Instr=00229393 | RD1=4  | RD2=5  | Imm=2    | ALUCtrl=001 | ALU=16 | Result=16 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=435000 | PC=000000bc | Instr=0013a023 | RD1=16 | RD2=8  | Imm=0    | ALUCtrl=000 | ALU=16 | Result=16 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=445000 | PC=000000c0 | Instr=00128293 | RD1=4  | RD2=8  | Imm=1    | ALUCtrl=000 | ALU=5  | Result=5  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=455000 | PC=000000c4 | Instr=fc62cae3 | RD1=5  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-5 | Result=-5 | Zero=0 | Branch=1 | PCSrc=1 |  |
| # t=465000 | PC=000000c8 | Instr=00418c63 | RD1=2  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=1 | PCSrc=0 |  |
| # t=475000 | PC=000000cc | Instr=00110133 | RD1=5  | RD2=8  | Imm=1    | ALUCtrl=000 | ALU=13 | Result=13 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=485000 | PC=000000d0 | Instr=404181b3 | RD1=2  | RD2=1  | Imm=1028 | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=495000 | PC=000000d4 | Instr=00229393 | RD1=5  | RD2=13 | Imm=2    | ALUCtrl=001 | ALU=20 | Result=20 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=505000 | PC=000000d8 | Instr=0023a023 | RD1=20 | RD2=13 | Imm=0    | ALUCtrl=000 | ALU=20 | Result=20 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=515000 | PC=000000dc | Instr=00420a63 | RD1=1  | RD2=1  | Imm=20   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=525000 | PC=000000e0 | Instr=00128293 | RD1=5  | RD2=8  | Imm=1    | ALUCtrl=000 | ALU=6  | Result=6  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=535000 | PC=000000e4 | Instr=fc62cae3 | RD1=6  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-4 | Result=-4 | Zero=0 | Branch=1 | PCSrc=1 |  |
| # t=545000 | PC=000000e8 | Instr=00418c63 | RD1=1  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=555000 | PC=000000ec | Instr=002080b3 | RD1=8  | RD2=13 | Imm=2    | ALUCtrl=000 | ALU=21 | Result=21 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=565000 | PC=000000f0 | Instr=004181b3 | RD1=1  | RD2=1  | Imm=4    | ALUCtrl=000 | ALU=2  | Result=2  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=575000 | PC=000000f4 | Instr=00229393 | RD1=6  | RD2=13 | Imm=2    | ALUCtrl=001 | ALU=24 | Result=24 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=585000 | PC=000000f8 | Instr=0013a023 | RD1=24 | RD2=21 | Imm=0    | ALUCtrl=000 | ALU=24 | Result=24 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=595000 | PC=000000fc | Instr=00128293 | RD1=6  | RD2=21 | Imm=1    | ALUCtrl=000 | ALU=7  | Result=7  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=605000 | PC=00000100 | Instr=fc62cae3 | RD1=7  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-3 | Result=-3 | Zero=0 | Branch=1 | PCSrc=1 |  |
| # t=615000 | PC=00000104 | Instr=00418c63 | RD1=2  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=1 | PCSrc=0 |  |
| # t=625000 | PC=00000108 | Instr=00110133 | RD1=13 | RD2=21 | Imm=1    | ALUCtrl=000 | ALU=34 | Result=34 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=635000 | PC=0000010c | Instr=404181b3 | RD1=2  | RD2=1  | Imm=1028 | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=645000 | PC=00000110 | Instr=00229393 | RD1=7  | RD2=34 | Imm=2    | ALUCtrl=001 | ALU=28 | Result=28 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=655000 | PC=00000114 | Instr=0023a023 | RD1=28 | RD2=34 | Imm=0    | ALUCtrl=000 | ALU=28 | Result=28 | Zero=0 | Branch=0 | PCSrc=0 |  |
| # t=665000 | PC=00000118 | Instr=00420a63 | RD1=1  | RD2=1  | Imm=20   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |  |
| # t=675000 | PC=0000011c | Instr=00128293 | RD1=7  | RD2=21 | Imm=1    | ALUCtrl=000 | ALU=8  | Result=8  | Zero=0 | Branch=0 | PCSrc=0 |  |

# Final Project

|            |             |                |        |        |          |             |        |           |        |          |         |
|------------|-------------|----------------|--------|--------|----------|-------------|--------|-----------|--------|----------|---------|
| # t=675000 | PC=00000048 | Instr=00128293 | RD1=7  | RD2=21 | Imm=1    | ALUCtrl=000 | ALU=8  | Result=8  | Zero=0 | Branch=0 | PCSrc=0 |
| # t=685000 | PC=0000004c | Instr=fc62cae3 | RD1=8  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-2 | Result=-2 | Zero=0 | Branch=1 | PCSrc=1 |
| # t=695000 | PC=00000020 | Instr=00418c63 | RD1=1  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |
| # t=705000 | PC=00000038 | Instr=002080b3 | RD1=21 | RD2=34 | Imm=2    | ALUCtrl=000 | ALU=55 | Result=55 | Zero=0 | Branch=0 | PCSrc=0 |
| # t=715000 | PC=0000003c | Instr=004181b3 | RD1=1  | RD2=1  | Imm=4    | ALUCtrl=000 | ALU=2  | Result=2  | Zero=0 | Branch=0 | PCSrc=0 |
| # t=725000 | PC=00000040 | Instr=00229393 | RD1=8  | RD2=34 | Imm=2    | ALUCtrl=001 | ALU=32 | Result=32 | Zero=0 | Branch=0 | PCSrc=0 |
| # t=735000 | PC=00000044 | Instr=0013a023 | RD1=32 | RD2=55 | Imm=0    | ALUCtrl=000 | ALU=32 | Result=32 | Zero=0 | Branch=0 | PCSrc=0 |
| # t=745000 | PC=00000048 | Instr=00128293 | RD1=8  | RD2=55 | Imm=1    | ALUCtrl=000 | ALU=9  | Result=9  | Zero=0 | Branch=0 | PCSrc=0 |
| # t=755000 | PC=0000004c | Instr=fc62cae3 | RD1=9  | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=-1 | Result=-1 | Zero=0 | Branch=1 | PCSrc=1 |
| # t=765000 | PC=00000020 | Instr=00418c63 | RD1=2  | RD2=1  | Imm=24   | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=1 | PCSrc=0 |
| # t=775000 | PC=00000024 | Instr=00110133 | RD1=34 | RD2=55 | Imm=1    | ALUCtrl=000 | ALU=89 | Result=89 | Zero=0 | Branch=0 | PCSrc=0 |
| # t=785000 | PC=00000028 | Instr=404181b3 | RD1=2  | RD2=1  | Imm=1028 | ALUCtrl=010 | ALU=1  | Result=1  | Zero=0 | Branch=0 | PCSrc=0 |
| # t=795000 | PC=0000002c | Instr=00229393 | RD1=9  | RD2=89 | Imm=2    | ALUCtrl=001 | ALU=36 | Result=36 | Zero=0 | Branch=0 | PCSrc=0 |
| # t=805000 | PC=00000030 | Instr=0023a023 | RD1=36 | RD2=89 | Imm=0    | ALUCtrl=000 | ALU=36 | Result=36 | Zero=0 | Branch=0 | PCSrc=0 |
| # t=815000 | PC=00000034 | Instr=00420a63 | RD1=1  | RD2=1  | Imm=20   | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=1 |
| # t=825000 | PC=00000048 | Instr=00128293 | RD1=9  | RD2=55 | Imm=1    | ALUCtrl=000 | ALU=10 | Result=10 | Zero=0 | Branch=0 | PCSrc=0 |
| # t=835000 | PC=0000004c | Instr=fc62cae3 | RD1=10 | RD2=10 | Imm=-44  | ALUCtrl=010 | ALU=0  | Result=0  | Zero=1 | Branch=1 | PCSrc=0 |
| # t=845000 | PC=00000050 | Instr=00000000 | RD1=0  | RD2=0  | Imm=0    | ALUCtrl=000 | ALU=0  | Result=0  | Zero=1 | Branch=0 | PCSrc=0 |

During each clock cycle, the processor performs the following operations:

1. The Program Counter (PC) points to the address of the current instruction in the Instruction Memory.
2. The instruction is fetched from memory using the current PC value.
3. The fetched instruction is decoded, and the source register addresses, destination register address, and immediate value are extracted.
4. The Control Unit generates the required control signals according to the instruction type.
5. The Register File reads the values of the source registers (RD1 and RD2).
6. The Immediate Generator produces the sign-extended immediate value when required.
7. The ALU performs the selected arithmetic or logical operation, and the result is generated.
8. For memory instructions, the ALU result is used as the memory address for reading or writing data.
9. The result is written back to the destination register if the instruction requires a write-back operation.
10. Finally, the next value of the Program Counter is determined:
  - $PC = PC + 4$  for normal sequential execution.
  - $PC = PC + \text{Immediate}$  when a branch instruction is taken (Branch = 1 and PCSrc = 1).

# Final Project

## 2. Final Register File and Data Memory

After program execution, the register file contains the expected final values. The data memory stores the Fibonacci sequence (1, 2, 3, 5, 8, 13, 21, 34, 55, 89), confirming the correct execution of arithmetic, memory, and control instructions.

```

Transcript

Final Register File


x0 = 0
x1 = 55
x2 = 89
x3 = 1
x4 = 1
x5 = 10
x6 = 10
x7 = 36

Final Data Memory

MEM[0] = 1
MEM[1] = 2
MEM[2] = 3
MEM[3] = 5
MEM[4] = 8
MEM[5] = 13
MEM[6] = 21
MEM[7] = 34
MEM[8] = 55
MEM[9] = 89

```

## 3. Waveform Verification

 

# Final Project

---

The waveform verifies the processor timing during execution. The clock controls synchronous operations, while memory locations are updated sequentially after each Store Word instruction. The waveform confirms the correct timing and functionality of the processor datapath.

## Conclusion

The simulation results verify the correct functionality of the proposed single-cycle RISC-V processor. All supported instructions were executed successfully, and the execution transcript, waveform, register file, and data memory contents matched the expected behavior, confirming the correctness of the processor design.